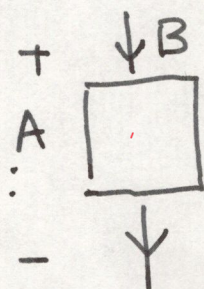


Modeling

A. Ideal Element




A across variable
B through variable

such that

$$\frac{AB^*}{2} = \text{Power}$$

Electrical Elements

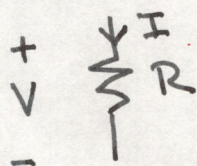


Laplace-domain

$$V = IR$$


time-domain

$$v = iR$$

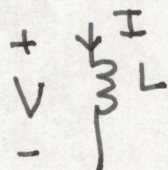

$$V = LsI$$

$$v = L \frac{di}{dt}$$

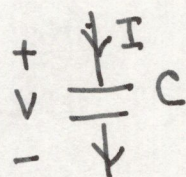


$$V = \frac{I}{Cs}$$

$$v = \frac{1}{C} \int i dt$$

Rectilinear Mechanical

A. The mass

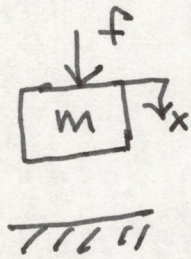

$$f = m \ddot{x}$$

$$\Downarrow$$

$$f = m \ddot{u}$$

x displacement from rest


u velocity

$$f u = \text{Power}$$

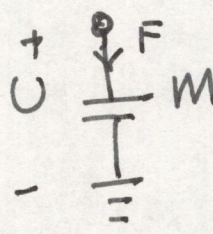(i) which is the across variable
F or $\dot{U}$?


(Ans) $\dot{U}$ due to consideration of the internal reference frame

$$f = m \ddot{u} \xrightarrow{\int} F = m \dot{U} \Rightarrow \boxed{\dot{U} = \frac{1}{m} F}$$



hence all Masses are fixed to ground!!


B. The Spring

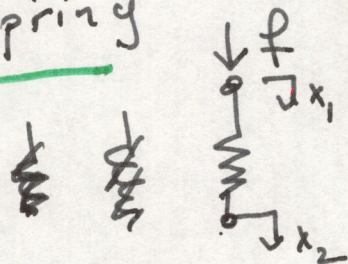


$$f = k(x_1 - x_2)$$

$$f = k \int (v_1 - v_2) dt$$
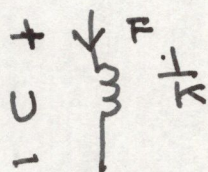
$$F = k \frac{1}{s} (v_1 - v_2) \Rightarrow [v_1 - v_2] = \boxed{\frac{s}{k} F = U}$$




C. The damper

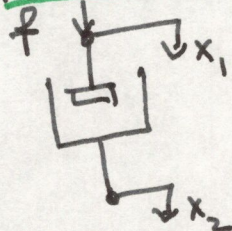

$$f = b(\dot{x}_1 - \dot{x}_2)$$


$$f = b(u_1 - u_2) \Rightarrow \boxed{F = bU}$$

$$\boxed{U = \frac{F}{b}}$$

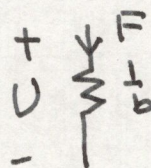

Example

given

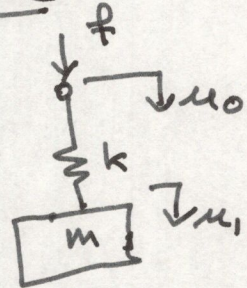


////

1. Find Electro-mech circuit with u is the across variable

Step 1:



Step 2:

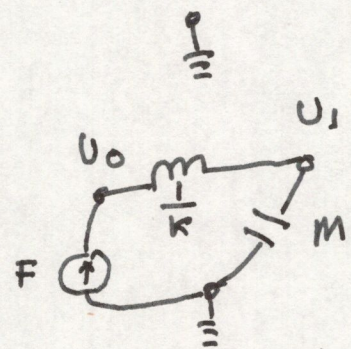

2. Find eqn of motion in Laplace domain

KCL

node U_0 : $F = \frac{U_0 - U_1}{\frac{s}{k}}$

node U_1 : $\frac{U_0 - U_1}{\frac{s}{k}} = \frac{U_1}{\frac{s}{m}}$

3. Find the governing ode's of the system

$$F = \frac{u_0 - u_1}{s/k} \Rightarrow sF = k[u_0 - u_1] \Rightarrow \boxed{\dot{p} = k[u_0 - u_1]} \quad (1)$$

$$\frac{u_0 - u_1}{\frac{s}{k}} = \frac{u_1}{\frac{1}{ms}} \Rightarrow k[u_0 - u_1] = Ms^2 u_1 \Rightarrow \boxed{k[u_0 - u_1] = M\ddot{u}_1} \quad (2)$$

4. Find the transfer function $\frac{U_1(s)}{U_0(s)}$

ie find $U_1(s)$ given $U_0(s)$

$$k[u_0 - u_1] = Ms^2 u_1 \quad \Leftarrow (2)$$

$\Downarrow$

$$k[u_0] = [ms^2 + k]u_1$$

$$\boxed{\frac{U_1}{U_0} = \frac{k}{ms^2 + k}}$$


$\swarrow$
 $\infty + k$

5. find asymp. behavior at


(a) $\omega \rightarrow 0$

(b) $\omega \rightarrow \infty$

Problem

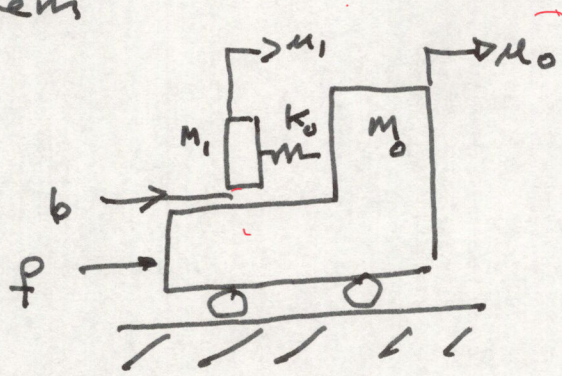

Problem

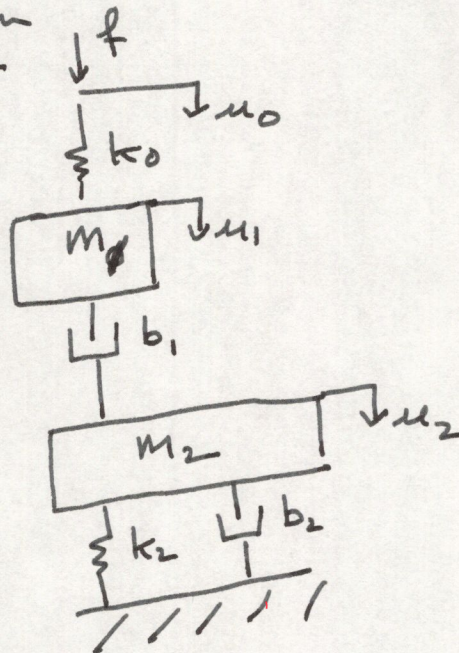

Find EM circuit
across variable

51

Problem

Given

